



Design of Digital Platforms

Exercise Session #2

Introduction to Gezel

Outline


- Register Transfer Level (RTL) hardware modeling
- GEZEL
 - Datapath
 - Controller
 - Testbench

Hardware Description

- Specific to implementation
 - Speed optimized
 - Area optimized
- Speed vs area trade off
- *Project Goal*: RSA coprocessor
 - Architectural possibilities:
 - Speed
 - Area
 - Flexibility



Register Transfer Level (RTL)

 - Above gate level
- Time abstracted to clock cycles



Register Transfer Level (RTL)

 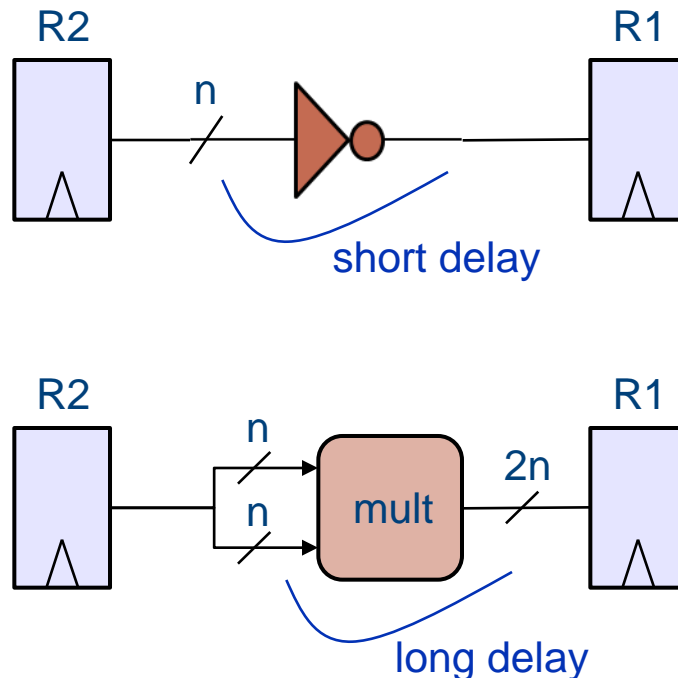
- Technology independent
- Number of logic operations per cycle is technology dependent
- **Critical path** depends on largest delay between two registers
 - Determines max clock frequency



RTL Computation

Computation steps happen in two phases:

 1. **Logic Computation** (Logic Function)
2. **Update** (Registers)




Language: GEZEL

- Many languages available for RTL Modeling: VHDL, Verilog, SystemC are mainstream.
- We use GEZEL
 - <http://rijndael.ece.vt.edu/gezel>
- Anything you write in GEZEL, you can also write in VHDL, Verilog, SystemC
- GEZEL can also be translated (automatically) into VHDL

Datapaths

Registers

 


reg $r : ns(n)$

Wires




sig $r : ns(n)$

Circuits

 

Expressions

Datapaths

 

```
reg r : ns(3);
```

```
reg v : ns(3);
```

```
sfg run {
```

```
    v = r + 1;
```

```
    r = v << 1;
```

```
}
```

Rules

```
sig b : ns(3);  
sfg do_always {  
  b = b + 1;  
}
```



RULES:

#1: No combinatorial loops between signals in a clock cycle

#2 Every output has to be assigned in each clock cycle

#3: A signal has to be assigned if used during a clock cycle

#4: Only one assignment during a clock cycle

GEZEL operators


Bitwise: $a \mid b$, $a \& b$, $a \wedge b$, $\sim a$

Selection: $s = a ? b : c$

Arithmetic: $a + b$, $a - b$, $a * b$, $-a$

Arithmetic: $a \ll n$, $a \gg n$

 Comparison: $a < b$, $a > b$, $a \leq b$, $a \geq b$, $a \neq b$, $a == b$



Controllers

- Generates *control signals*
 - Multiplexing
 - Register update enable
- Datapath is useless without the controller
- Two types:
 - Combinatorial (Hardwired)
 - Finite State Machine with Datapath (FSMD)

Controllers: Hardwired

```
dp example1( in a_in, b_in, c_in : ns(1);  
              out result : ns(1))  
{  
  
    sfg run {  
        result = (a & b) ^ c;  
    }  
}
```

```
hardwired hw_control(example1){run;}
```

Controllers - Finite State Machine with Datapath (1)


Basic idea: Controller and datapath exist in two separate modules.

Controller:

- State-machine
- Controls the program flow

Datapath:

- Performs data processing operations

 

Controllers - Finite State Machine with Datapath (2)

```
dp count(in a_in : ns(10); out result : ns(10)) {  
  reg a_reg : ns(10);  
  sfg load {  
    a_reg = a_in;  
  }  
  sfg work {  
    a_reg = (a_reg < 999) ? (a_reg + 1) : 0;  
  }  
  ...  
}
```

```
fsm ctl_count(count) {  
  initial s0;  
  state s1;  
  @s0 (load) -> s1;  
  @s1 (work) -> s1;  
}
```

See: fsmd.fdl

Controllers - Finite State Machine with Datapath (3)

Tips for writing FSMDs:

- Avoid writing multiplexers ($a ? b : c$) inside the state machine
- Data processing and control sequencing should be separated

Simulation Directives

\$display(arg, ..)

Used inside of an sfg.
Prints strings, expressions and meta-variables.

\$cycle

Used as a \$display argument.
Returns current clock cycle (first cycle = 1).

\$sfg

Used as a \$display argument.
Returns the name of the current sfg.

\$dp

Used as a \$display argument.
Returns the name of the current datapath.

\$finish

Used inside of an sfg .
Aborts the simulation.

Simulation

- **fdlsim**

fdlsim [d] [<design.fdl>] <cyclecount>

 termination :


- a. target cycle count is reached
- b. runtime error
- c. \$finish directive is executed

- **-d: debug mode**

Example: fdlsim counter.fdl 20

Test Bench

Only used for simulation

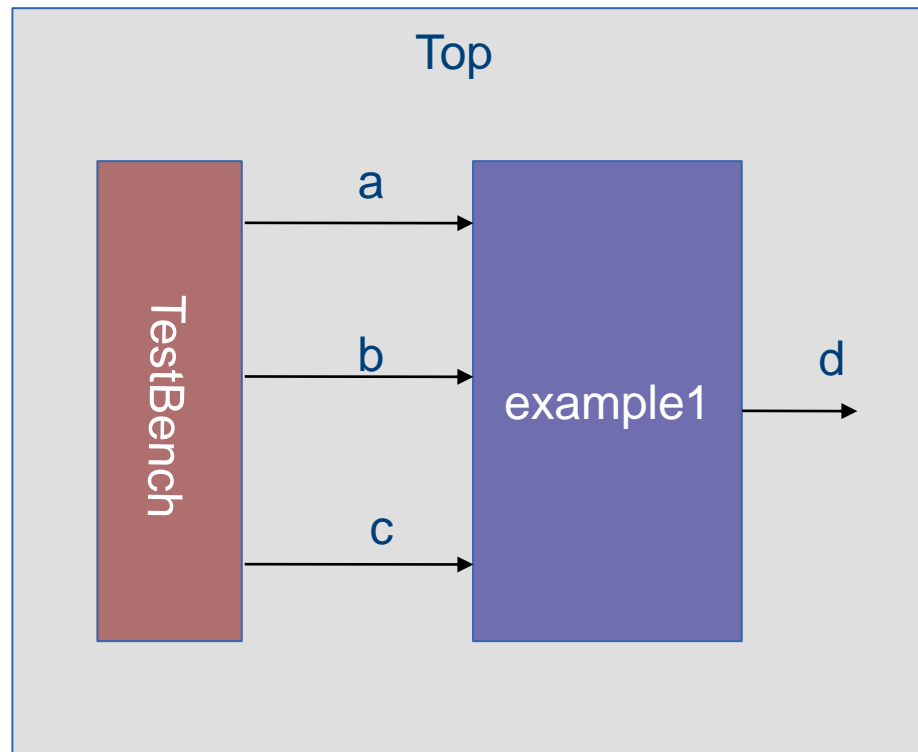

Test bench

```
dp TestBench( out a_out,  
               b_out,  
               c_out :ns(1))  
  
{  
  sfg run{  
    a_out = 0b1;  
    b_out = 0b1;  
    c_out = 0b0;  
  }  
}
```

```
system s{  
  top;  
}
```

```
hardwired hw_control(TestBench){run;}
```

```
dp top(){  
  sig a,b,c,d :ns(1);  
  
  use TestBench(a,b,c);  
  use example1(a,b,c,d);  
}
```

See: testbench.fdl